

EE520 Design of Digital Systems

Subject: Project 2 enhancing project 1 with XOR, rising edge triggered D Flip Flop and Full adder

Name : Zeyar Win

Course: Design of Digital Systems

Library : zxw_lib

Design constraint library with NMOS 8 lambda/2 lambda, PMOS being 16 lambda/2 lambdas twice the size of NMOS. The design of transistors is unskewed. The design is vertical as in tutorial 1 which was done in the first week of the class. The CMOS is used for multiplexer. AOI is implemented according to those above specifications in project 1. In project 2, XOR, rising edge triggered d flip flop and full adder is implemented. XOR implementation is simple since project 1 introduces the use of layout virtuoso software, and inverter, NAND, NOR, AOI and 2 to 1 multiplexer gates are successfully implemented before this project 2. XOR is tested with timing simulation diagram. The full adder can be tested using BSTEST simulation. D flip flop can be tested looking at output changes as input in timing simulation diagram only when clock goes from zero to one. The full adder in the project is finished routing cells being minimized and following the routing channel height guidelines 26 lambdas at top and bottom, and 52 lambdas between rows. For full adder, 52 lambdas between rows do not need to be considered.

For inverter, NMOS is 2.4um and PMOS is 4.8um. Using this as reference, NAND NMOS is 4.8um and PMOS is 4.8um. The equations for transistor sizing are $W=1/R$ and R of PMOS = $2R$ of NMOS. Only look at the worst case of transistors to do sizing. For the parallel transistors case, the worst case is when only one transistor is on while for transistors in series, all transistors have to be on. As similar to calculating NAND, NOR NMOS is 2.4um for NMOS and

9.6um for PMOS. NMOS is minimum size which is 2.4um. To calculate PMOS, $[1/(1/W_p + 1/W_p)]$ being equal to 4.8 is used.

Project 2 layouts were minimized as possible to fit in corner cell. Finger transistors were not used in this project and sizing of PMOS and NMOS was not huge. Thus, there was not much concern in this project about fitting the implemented layouts cells in corner cell. Layouts were minimized as much as possible to decrease parasitic capacitances. From BSTEST layout, it can be clearly seen that the layout of this project is using less than 70% of all available spacing.

Timing diagram should be simulated first to check functionality of schematic. In this project, Layout of multiplexer logic failed. This delayed ability to finish project completely in time. The d flip flop and multiplexer were fixed in time although BSTEST layouts were not completed in time.


The project 1 was finished in time without cell sizes minimized to the most minimum size. There was problem with server for waveform simulation right before project was due. It could be expected in industry. It is employee's responsibility to start work early and finish in time; it also depends on manager's leniency on deadline. Project 1 cell layouts were later corrected to most minimum size being optimized to decrease time delay, decrease parasitic capacitance and increase performance. When doing layout, pins names should be capital letters which are industry standard. In this project, this was accidentally ignored; the finishing layouts and simulation was first priority. The later optimization of project 1 cells took some time away from finishing project 2. Since finger transistors were not used in project 1, there was little space for two contacts in the middle of cells after minimizing cells and had difficulty in putting two contacts for inputs and outputs. 1 week was spent on moving the NMOS and PMOS around until the poly was noticed that it could pass through metal 1 of ground without shorting the cells. The poly didn't move contacts of the metal 1 in both ground and Vdd. The DRC and LVS clean of the layout confirm the validity of using poly passing through ground metal.

For project 2, the timing simulation of XOR is similar to project 1 simulation. Matching the truth logic of gate with the simulation diagram verify the functionality of XOR. Propagation delay is extracted by observing the timing delay difference between 50% of output and 50% of input assuming other inputs are constant. For DFF simulation, in addition to the logic verification, the minimum pulse width of clock 1 and clock 2, and the guard time were observed and included in lab report. The BSSUM simulation needed more time and could not be included in this lab report. The simulation needed manual timing inputs with careful consideration.

These projects take a lot of time. The layouts being minimized as much as possible when not familiar with the tools are hard. The layouts are relatively easily minimized when tools become familiar as time goes on although it takes time and effort. Project 1 layouts are at the

best situation. If the layouts were to be implemented again, the poly connecting input or output contacts would not pass through the ground and VDD metals. There will be other ways to do it although it will take more time. Pin names will be changed to capital letters. For improving project 2, BSSUM simulation could be finished considering more time is available and not a lot of other classes work. Project 2 layouts were optimized. All project 1 and 2 cell layouts are completed successfully without DRC and LVS errors and warnings.



Cell Name:	Zxw_inv	
Function/Truth Table:		
A	Y	
0	1	
1	0	
Propagation Delay:		

 


Layout 374.4 μm^2

A **Y ↑** **.342ns**

A **Y ↓** **.28ns**

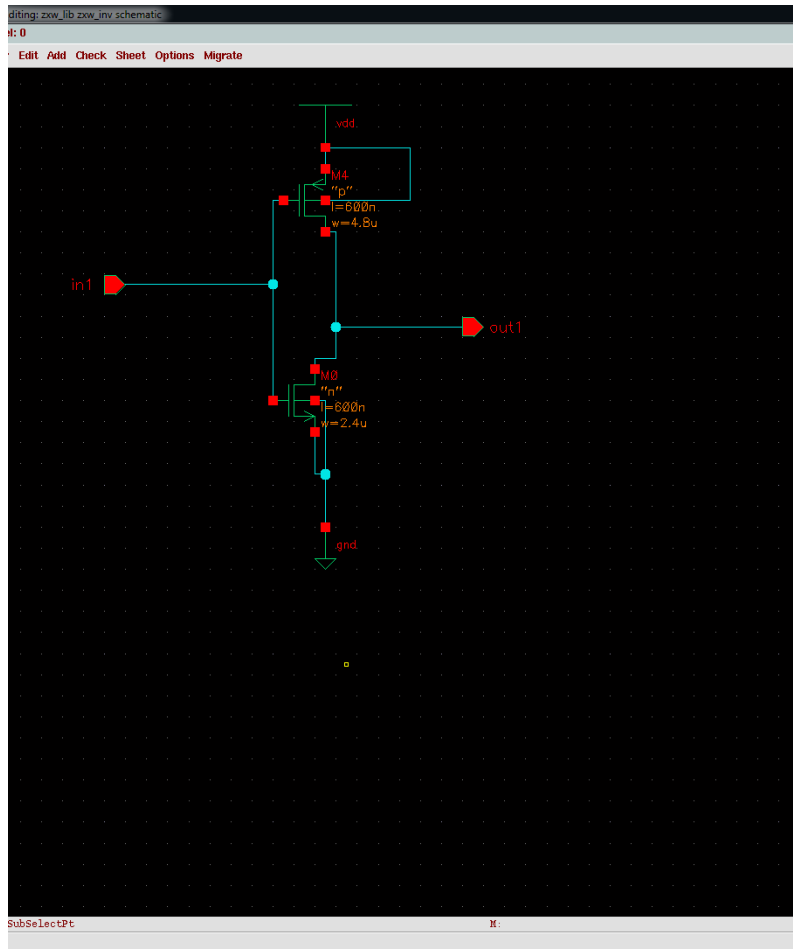 

 

```
//Verilog HDL for "zxw_lib", "zxw_inv" "zxw_inv"
```

```
module zxw_inv ( out1, in1 );
```

```
    output out1;
```

```
    input in1;
```

```
    not(out1,in1);
```

```
endmodule
```

```
~
```

```
~
```


```

zxw_inv.sp = (~/ee620) - GVIEW
File Edit Tools Syntax Buffers Window Help
[Icons: Folder, Disk, Floppy, Printer, Undo, Redo, Copy, Paste, Find, Run, Previous, Next, Settings]


M0      out1#3  in1#6  gnd!#3  gnd!#1  nmos  L=0.6  W=2.4
+ AD=3.89  AS=4.045  PD=6.4  PS=6.5
M4      out1#4  in1#4  vdd!#3  vdd!#1  pmos  L=0.6  W=4.8
+ AD=6.57  AS=6.57  PD=8    PS=8
*
*
*      RESISTOR AND CAP/DIODE CARDS
*
Re1      in1#4  in1#5      391.9460
Re2      in1#5  in1#1      19.2000
Re3      in1#5  in1#6      249.4459
Rc1      in1#1  in1#2      20.5000
Rc2      out1#1  out1#2      0.5433
Rc3      out1#2  out1#3      26.8841
Rc4      out1#2  out1#4      20.9163
Rc5      gnd!   gnd!#2  1.240E-02
Rc6      gnd!#2  gnd!#3  26.9329
Rc7      gnd!#1  gnd!#2  14.2857
Rc8      vdd!#2  vdd!     1.728E-02
Rc9      vdd!   vdd!#3  20.4560
Rc10     vdd!#1  vdd!#2  10.0000
Rb1      in1    in1#2      0.5000
Rb2      out1#1  out1     0.5000
*
*      CAPACITOR CARDS
*
C1      out1    vdd!     1.222E-16
C2      in1#5   gnd!#1  5.743E-16
C3      out1#2  gnd!#1  2.843E-16
C4      out1#4  in1#5   5.198E-17
C5      gnd!#3  out1#3  1.069E-16
C6      out1    gnd!#1  3.653E-16
C7      out1    vdd!#1  2.474E-16
C8      out1#4  in1#4   1.877E-16
C9      vdd!#1  in1#4   3.898E-17
C10     in1#6   gnd!#1  3.531E-16
C11     vdd!#3  in1#4   1.776E-16
C12     in1#1   gnd!#1  7.440E-16
C13     out1#3  in1#6   9.305E-17
C14     gnd!#3  in1#5   7.055E-18
C15     out1#1  gnd!#1  3.668E-16
C16     gnd!#3  in1#6   1.032E-16
C17     out1#2  in1#6   2.143E-17
C18     in1#1   gnd!#3  2.116E-17
C19     out1#2  in1#5   2.814E-16
C20     in1#1   out1#2  3.521E-17
C21     vdd!#1  gnd!#1  1.899E-16

```


Library Name:			Zxw_lib	
Cell Name:			Zxw_mux2	
Function/Truth Table:				
S A1 A0			Y	
0 0 0			0	
0 0 1			0	
0 1 0			1	
0 1 1			1	
1 0 0			0	
1 0 1			1	
1 1 0			0	
1 1 1			1	
A1	Y ↑	.473n		
A1	Y↓	.507ns		
A0	Y ↑	.383n		
A0	Y↓	.442n		
S	Y ↑	.322n		
S	Y↓	.372n		
Symbol with Port Names:				

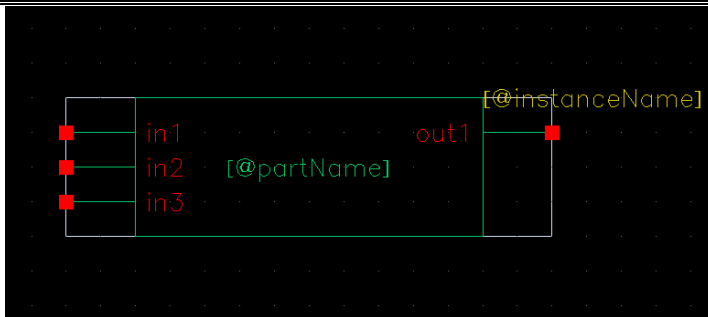

Schematic:

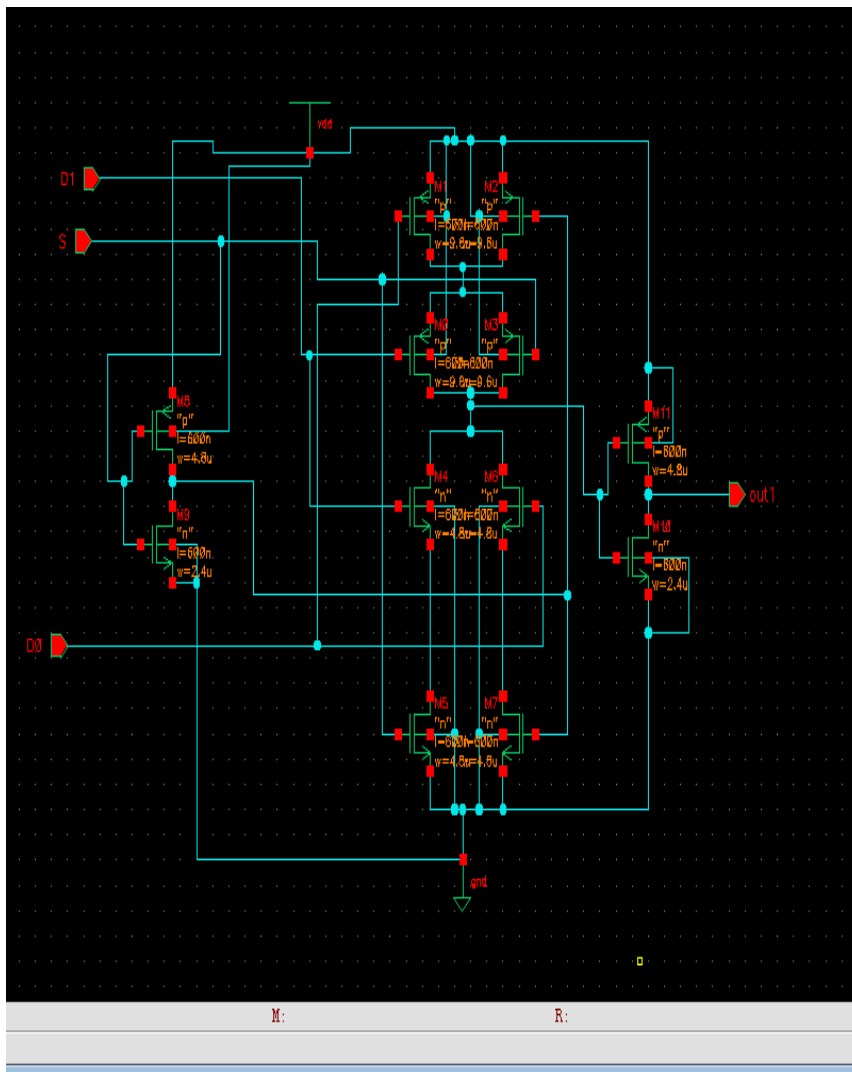

Layout:

 

Layout 748.8 μm^2

Verilog Model:

```
module zxc_mux2 (in1,in2,in3,in4,out1);
```

```
    Input in1;
```

```
    Input in2;
```

```
    Input in3;
```

```
    Input in4;
```

```
output out1;
```

and(a1, in1,in2);

and (a2,in3,in4);

or(a3,a1,a2);

endmodule

Comments/Notes:

*


*Parasitic capacitance sheets

```
zxcw_mux2.sp = (~/ee620) - GVIEW
File Edit Tools Syntax Buffers Window Help
[Icons]
.SUBCKT zxcw_mux2 vdd! gnd! D0 D1 S out1
*
*
* caps2d version: 7
*
*
* TRANSISTOR CARDS
*
M6 net29#2 D0#5 net41 gnd!#2 nmos L=0.6 W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M7 net41 net49#4 gnd!#4 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M5 net33 S#6 gnd!#4 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M4 net29#3 D1#5 net33 gnd!#2 nmos L=0.6 W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M9 net49#6 S#5 gnd!#1 gnd!#2 nmos L=0.6 W=2.4
+ AD=4 AS=2.24 PD=6.6 PS=2.3
M10 out1#1 net29#10 gnd!#1 gnd!#2 nmos L=0.6 W=2.4
+ AD=4 AS=2.24 PD=6.6 PS=2.3
M1 net8 D0#4 vdd!#4 vdd!#2 pmos L=0.6 W=9.6
+ AD=12.48 AS=7.2 PD=12.2 PS=1.5
M2 net8#3 net49#3 vdd!#4 vdd!#2 pmos L=0.6 W=9.6
+ AD=7.2 AS=7.2 PD=1.5 PS=1.5
M3 net29#7 S#7 net8#3 vdd!#2 pmos L=0.6 W=9.6
+ AD=7.2 AS=7.2 PD=1.5 PS=1.5
M0 net29#7 D1#6 net8#5 vdd!#2 pmos L=0.6 W=9.6
+ AD=7.2 AS=12.48 PD=1.5 PS=12.2
M8 net49#7 S#3 vdd!#1 vdd!#2 pmos L=0.6 W=4.8
+ AD=6.79 AS=3.875 PD=8.4 PS=2
M11 out1#3 net29#12 vdd!#1 vdd!#2 pmos L=0.6 W=4.8
+ AD=6.79 AS=3.875 PD=8.4 PS=2
*
*
* RESISTOR AND CAP/DIODE CARDS
*
Re1 D0#4 D0#2 362.9682
Re2 D0#2 D0#5 176.9445
Re3 net49#3 net49#2 340.5209
Re4 net49#2 net49#4 195.0167
Re5 D1#2 D1#4 82.3619
Re6 D1#4 D1#5 208.6583
Re7 D1#4 D1#6 386.0417
Re8 S#3 S#4 311.6037
Re9 S#4 S#5 281.1132
Re10 S#5 S#6 839.5580
Re11 S#4 S#2 23.1818
```


--

Library Name:		
Cell Name:	Zxw_nand2	
Function/Truth Table:		
0 0	1	
0 1	1	
1 0	1	
1 1	0	
Propagation Delay:		
A Y↑	.310ns	
A Y↓	.426n	
B Y↑	.384ns	
B Y↓	.390ns	


Symbol with Port Names:

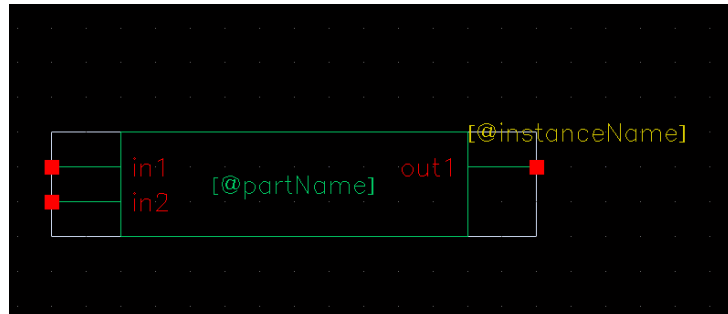

Schematic:

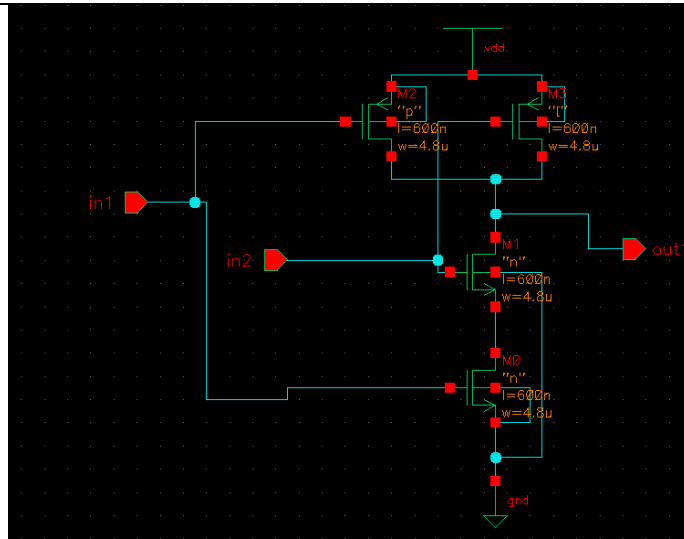

Layout:

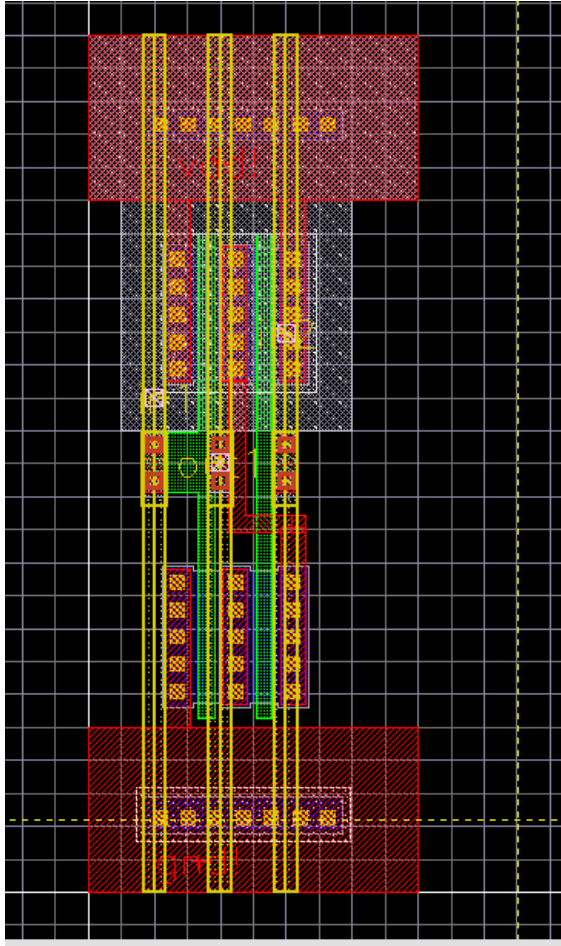

Layout 374.4 μm^2

Verilog Model:

```
module zxw_nand (in1,in2,out1 );
```

```
    input in1;
```

```
    input in2;
```

```
    output out1;
```

```
    nand(out1,in1,in2);
```

```
endmodule
```


```
.SUBCKT zxw_nand2 vdd! gnd! in1 in2 out1
*
* caps2d version: 7
*
* TRANSISTOR CARDS
*
M2      out1#3  in2#3  net4      gnd!#1  nmos    L=0.6  W=4.8
+ AD=6.57  AS=3.765 PD=8      PS=1.8
M3      net4    in1#6  gnd!#2    gnd!#1  nmos    L=0.6  W=4.8
+ AD=3.765 AS=6.57 PD=1.8    PS=8
M0      out1#5  in1#4  vdd!#4    vdd!#2  pmos    L=0.6  W=4.8
+ AD=3.765 AS=6.57 PD=1.8    PS=8
M1      out1#5  in2#4  vdd!#1    vdd!#2  pmos    L=0.6  W=4.8
+ AD=3.765 AS=6.57 PD=1.8    PS=8
*
* RESISTOR AND CAP/DIODE CARDS
*
Re1      in1#4  in1#5      264.9745
Re2      in1#5  in1#1      21.8182
Re3      in1#5  in1#6      312.4745
Re4      in2#1  in2#2      26.6667
Re5      in2#2  in2#3      294.4413
Re6      in2#2  in2#4      244.4413
Rc1      in1#1  in1#2      20.5000
Rc2      in2#5  in2#1      0.5000
Rc3      out1#3  out1#4     16.9026
Rc4      out1#4  out1#1     1.159E-02
Rc5      out1#4  out1#5     20.6351
Rc6      vdd!#1  vdd!#3     20.4591
Rc7      vdd!#3  vdd!      1.274E-02
Rc8      vdd!   vdd!#4     20.4579
Rc9      vdd!#2  vdd!#3     11.4286
Rc10     gnd!#1  gnd!      14.3091
Rc11     gnd!   gnd!#2     16.3670
Rb1      in1#3  in1#2      0.5000
Rb2      out1#1  out1      1.0000
Rb3      in2#6  in2#5      0.5000
Ra1      in1    in1#3      0.1175
Ra3      in2    in2#6      0.2350
*
* CAPACITOR CARDS
*
C1      out1#3  in2#2      6.475E-17
```

--


Library Name:	
Cell Name:	Zxw_nor
Function/Truth Table:	
f0 0	1
0 1	0
1 0	0
1 1	0

Propagation Delay:	
A Y↑	.36ns
A Y↓	.29ns
B Y↑	.2529ns
B Y↓	.31ns


Symbol with Port Names:

 

Schematic:

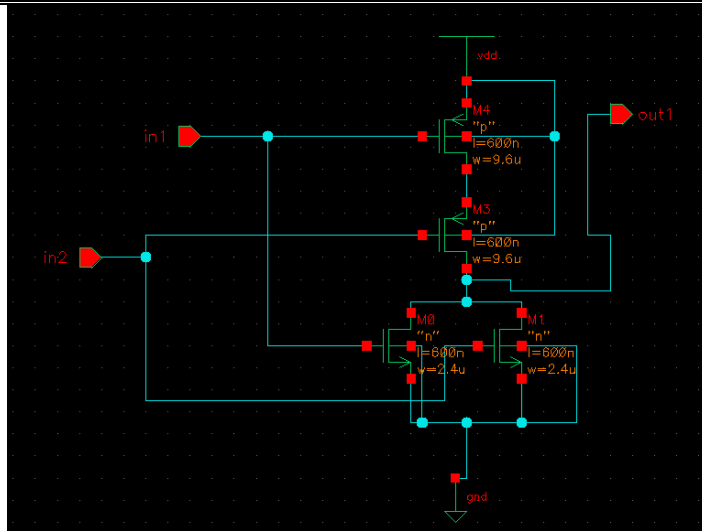

Layout:

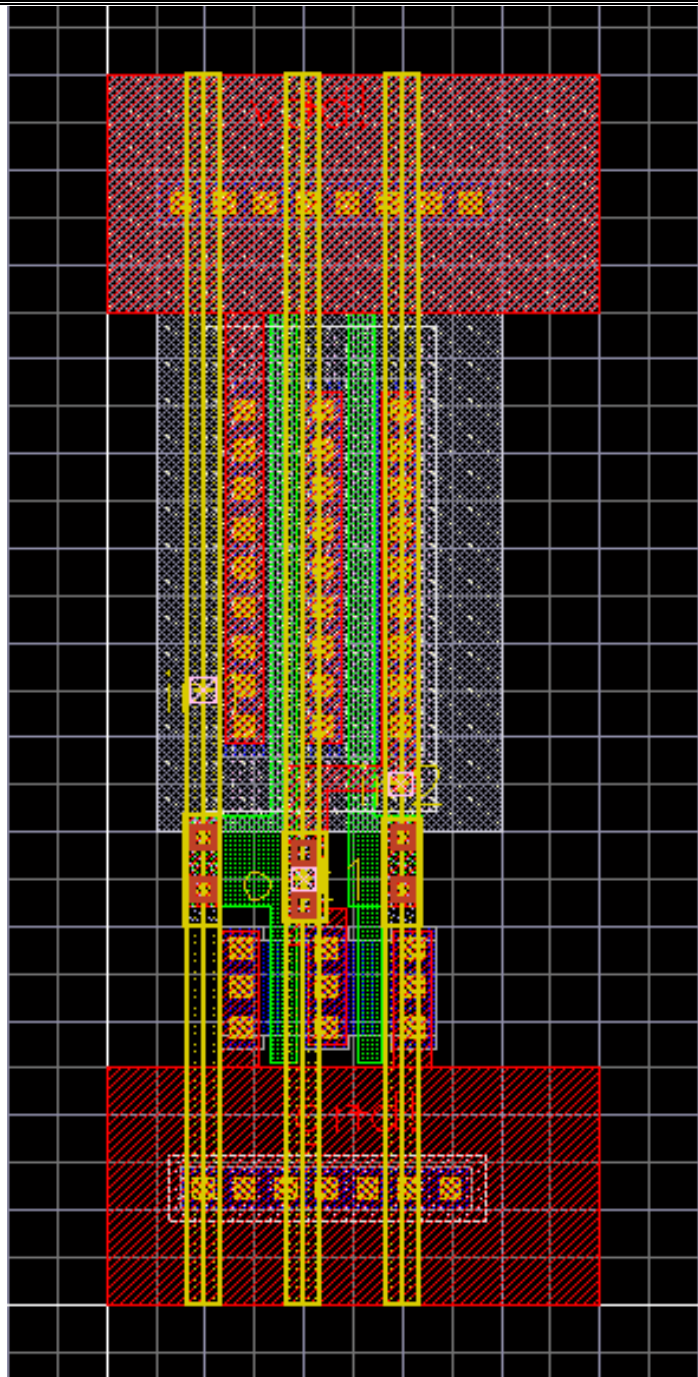

Layout 374.4 μm^2

```

zxc_nor2.sp = (~/ee620) - GVIEW1
File Edit Tools Syntax Buffers Window Help
[Icons: Folder, Disk, Floppy, Printer, Undo, Redo, Copy, Paste, Find, Run, Previous, Next]

.SUBCKT zxc_nor2 vdd! gnd! in1 in2 out1
*
*
* caps2d version: 7
*
*
* TRANSISTOR CARDS
*
M1 out1#4 in2#4 gnd!#1 gnd!#2 nmos L=0.6 W=2.4
+ AD=2.185 AS=3.89 PD=2.2 PS=6.4
M0 out1#4 in1#6 gnd!#4 gnd!#2 nmos L=0.6 W=2.4
+ AD=2.185 AS=3.89 PD=2.2 PS=6.4
M3 out1#3 in2#3 net29 vdd!#1 pmos L=0.6 W=9.6
+ AD=11.52 AS=6.24 PD=12 PS=1.3
M4 net29 in1#4 vdd!#3 vdd!#1 pmos L=0.6 W=9.6
+ AD=6.24 AS=12.48 PD=1.3 PS=12.2
*
*
* RESISTOR AND CAP/DIODE CARDS
*
Re1 in1#4 in1#5 367.2919
Re2 in1#5 in1#1 21.5217
Re3 in1#5 in1#6 154.7919
Re4 in2#1 in2#2 29.1304
Re5 in2#2 in2#3 349.4290
Re6 in2#2 in2#4 140.2702
Rc1 in1#1 in1#2 20.5000
Rc2 out1#3 out1#1 12.0720
Rc3 out1#1 out1#4 26.8997
Rc4 in2#5 in2#1 0.5000
Rc5 gnd!#1 gnd! 26.9210
Rc6 gnd! gnd!#3 1.063E-02
Rc7 gnd!#3 gnd!#4 26.9347
Rc8 gnd!#2 gnd!#3 14.2857
Rc9 vdd!#2 vdd! 1.735E-02
Rc10 vdd! vdd!#3 11.7920
Rc11 vdd!#1 vdd!#2 10.0000
Rb1 in1#3 in1#2 0.5000
Rb2 out1#1 out1 1.0000
Rb3 in2#6 in2#5 0.5000
Ra1 in1 in1#3 0.2175
Ra3 in2 in2#6 0.1000
*
* CAPACITOR CARDS
*
C1 out1#1 gnd!#1 1.568E-17

```

Verilog Model:

```
module zxw_nor ( in1,in2,out1);  
  
    input in1;  
  
    input in2;  
  
    output out1;  
  
    nor(out1,in1,in2);  
  
endmodule
```



.

Library Name:		
Cell Name:	Zxw_aoi	
Function/Truth Table:		
0000		1
0001		1
0010		1
0011		0
0100		1
0101		1
0110		1

0111	0
1000	1
1001	1
1010	1
1011	0
1100	0
1101	0
1110	0
1111	0
Propagation Delay:	
A0 Y↑	.370ns
A0 Y↓	.545ns
A1 Y↑	.397ns
A1 Y↓	.541ns
B0 Y↑	.712ns


B0 Y↓	.375ns
B1 Y↑	.339ns
B1 Y↓	.374ns

Symbol with Port Names:

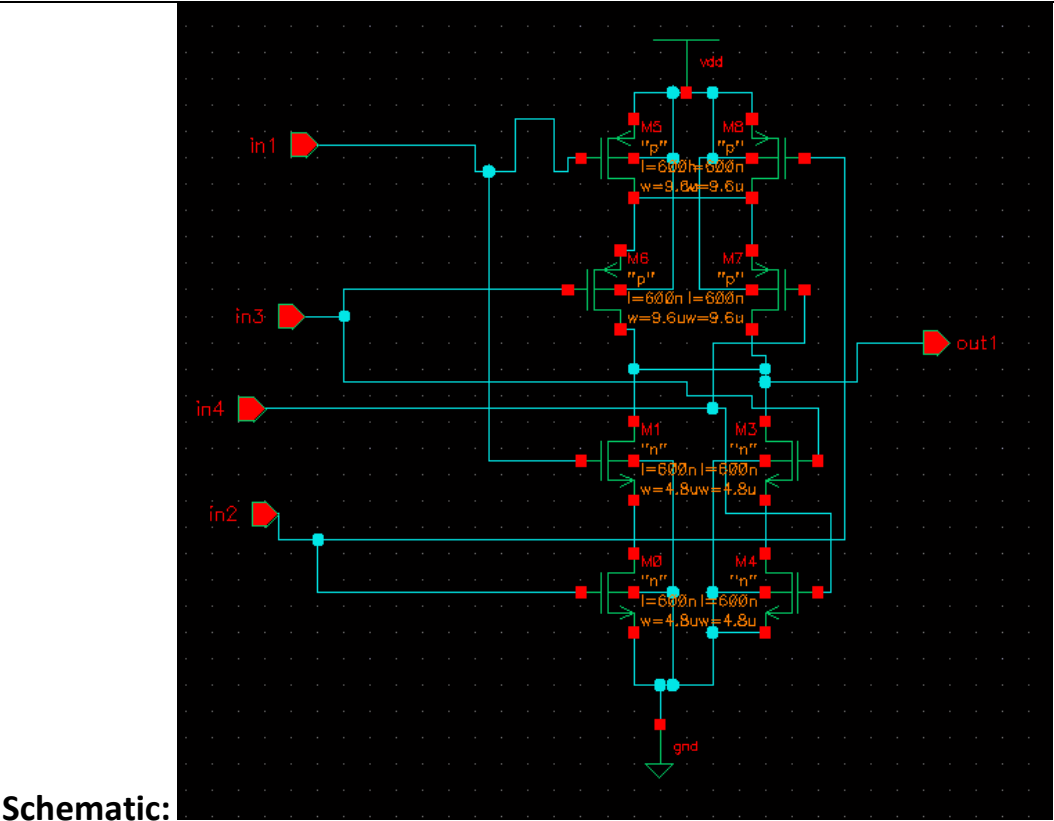 

Schematic:

Layout:

 

Layout 599.04 um²

Verilog Model:

```
module zxcw_aoi (in1,in2,in3,in4,out1 );  
  
    input in1;  
  
    input in2;  
  
    input in3;  
  
    input in4;  
  
    output out1;  
  
    and(a,in1,in2);
```



```
and(b,in3,in4);
```

```
or(c,a,b);
```

```
not(out1,c);
```

```
endmodule
```

zxw_aoi2.sp = (~/ee620) - GVIEW



File Edit Tools Syntax Buffers Window Help

.SUBCKT zxw_aoi2 vdd! gnd! in1 in2 in3 in4 out1

*
*
* caps2d version: 7
*
*
* TRANSISTOR CARDS
*
*
M0 net33#4 in2#5 gnd!#1 gnd!#2 nmos L=0.6 W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M4 net21 in4#3 gnd!#1 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M3 out1#4 in3#2 net21 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M1 out1#4 in1#5 net33#2 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.765 AS=6.57 PD=1.8 PS=8
M5 net12 in1#4 vdd!#4 vdd!#2 pmos L=0.6 W=9.6
+ AD=6.24 AS=11.52 PD=1.3 PS=12
M6 out1#3 in3#1 net12 vdd!#2 pmos L=0.6 W=9.6
+ AD=6.24 AS=6.24 PD=1.3 PS=1.3
M7 out1#3 in4#1 net12#3 vdd!#2 pmos L=0.6 W=9.6
+ AD=6.24 AS=6.24 PD=1.3 PS=1.3
M8 net12#3 in2#6 vdd!#1 vdd!#2 pmos L=0.6 W=9.6
+ AD=6.24 AS=11.52 PD=1.3 PS=12
*
*
* RESISTOR AND CAP/DIODE CARDS
*
*
Re1 in1#4 in1#1 418.3636
Re2 in1#1 in1#5 262.3004
Re3 in4#1 in4#2 305.9051
Re4 in4#2 in4#3 174.5000
Re5 in2#1 in2#4 30.9091
Re6 in2#4 in2#5 186.1363
Re7 in2#4 in2#6 328.9197
Re8 in3#1 in3#2 556.0237
Re9 in3#2 in3#3 694.7712
Rc1 in1#1 in1#2 20.5000
Rc2 net33 net33#2 17.0944
Rc3 net12 net12#2 12.3944
Rc4 out1#3 out1#1 11.7946
Rc5 out1#1 out1#4 16.2544
Rc6 in4#4 in4#2 20.5000
Rc7 net12#3 net12#4 12.3944
Rc8 net33#3 net33#4 16.0944
Rc10 in3#3 in3#4 0.5000
Rc11 vdd!#1 vdd!#3 11.6769

Cell Name:	Zxw_fa	
Function/Truth Table:		
A B Cin	Cout Y	
0 0 0	0 0	
0 0 1	1 0	
0 1 0	1 0	
0 1 1	1 0	
1 0 0	0 1	
1 0 1	0 1	
1 1 0	0 1	
1 1 1	1 1	
A Sum ↑	1.304ns	
A Sum ↓	1.055ns	
B Sum↑	.964ns	

B Sum ↓	1.03ns
Cin Sum ↑	.501ns
Cin Sum ↓	.455ns
A Cout ↑	.745ns
A Cout ↓	.748ns
B Cout ↑	.678ns
B Cout ↓	.274ns
Cin Cout ↑	.673ns
Cin Cout ↓	.251ns

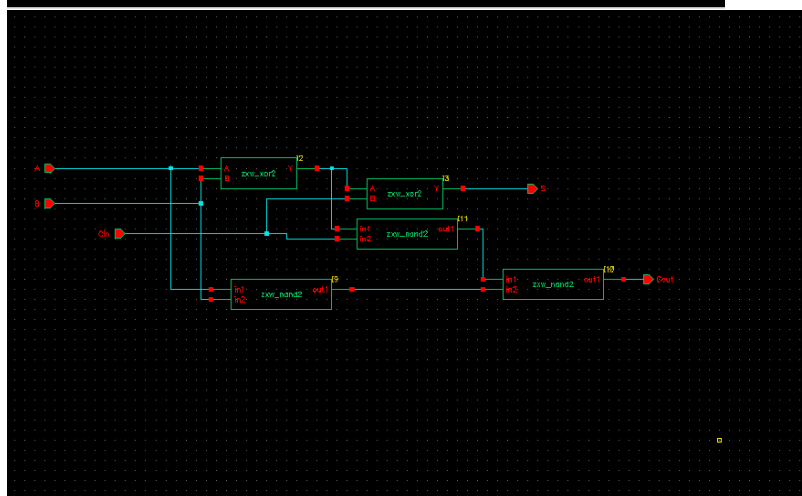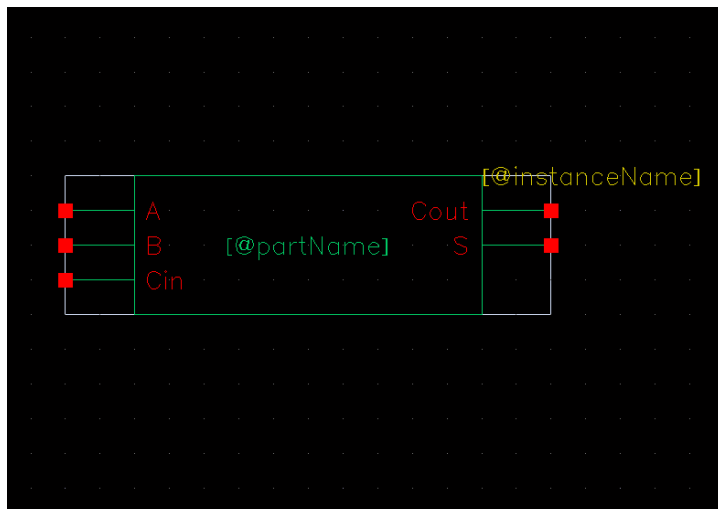

```
module zxw_fa ( Cout, S, A, B, Cin );
```

```
input Cin;
```

```
output S;
```

```
input A;
```

```
output Cout;
```

```
input B;
```

```
xor(C,A,B);
```

```
xor(S,C,Cin);
```

```
nand(D,C,Cin);
```

```
nand(E,A,B);
```

```
nand(Cout,E,D);
```


```
endmodule
```





```
zxw_fa.sp = (~/ee620) - GVIEW
File Edit Tools Syntax Buffers Window Help
*
.SUBCKT zxw_fa vdd! gnd! A B Cin Cout SUM
*
* caps2d version: 7
*
* TRANSISTOR CARDS
*
MI6/M11 gnd!#19 net20#12 I6/net1#2 gnd!#1 nmos L=0.6
+ W=2.4
+ AD=4.11 AS=4.11 PD=6.8 PS=6.8
MI6/M7 SUM#5 net20#13 I6/net16#2 gnd!#1 nmos L=0.6 W=4.8
+ AD=3.93 AS=6.9 PD=2.1 PS=8.6
MI6/M5 I6/net17#2 I6/net1#6 SUM#5 gnd!#1 nmos L=0.6 W=4.8
+ AD=6.9 AS=3.93 PD=8.6 PS=2.1
MI6/M8 gnd!#18 Cin#3 I6/net16#4 gnd!#1 nmos L=0.6 W=4.8
+ AD=3.93 AS=6.9 PD=2.1 PS=8.6
MI6/M6 I6/net17#4 I6/net5#2 gnd!#18 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.9 AS=3.93 PD=8.6 PS=2.1
MI6/M9 I6/net5#4 Cin#8 gnd!#17 gnd!#1 nmos L=0.6 W=2.4
+ AD=4.11 AS=4.11 PD=6.8 PS=6.8
MI5/M11 gnd!#22 A#15 I5/net1#2 gnd!#1 nmos L=0.6 W=2.4
+ AD=4.11 AS=4.11 PD=6.8 PS=6.8
MI5/M7 net20#4 A#16 I5/net16#2 gnd!#1 nmos L=0.6 W=4.8
+ AD=3.93 AS=6.9 PD=2.1 PS=8.6
MI5/M5 I5/net17#2 I5/net1#6 net20#4 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.9 AS=3.93 PD=8.6 PS=2.1
MI5/M8 gnd!#21 B#10 I5/net16#4 gnd!#1 nmos L=0.6 W=4.8
+ AD=3.93 AS=6.9 PD=2.1 PS=8.6
MI5/M6 I5/net17#4 I5/net5#2 gnd!#21 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.9 AS=3.93 PD=8.6 PS=2.1
MI5/M9 I5/net5#4 B#15 gnd!#20 gnd!#1 nmos L=0.6 W=2.4
+ AD=4.11 AS=4.11 PD=6.8 PS=6.8
MI4/M2 Cout#4 net14#10 I4/net4 gnd!#1 nmos L=0.6 W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
MI4/M3 I4/net4 net11#13 gnd!#15 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=3.765 AS=6.57 PD=1.8 PS=8
MI3/M2 net11#4 net20#20 I3/net4 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
```

Cell Name:	Zxw_xor	
Function/Truth Table:		
A1 A0		Y
0 0		0

0 1	1
1 0	1
1 1	0
B Y↑	. 568 ns
B Y↓	. 536 ns
A Y↑	. 548ns
A Y↓	.534 ns

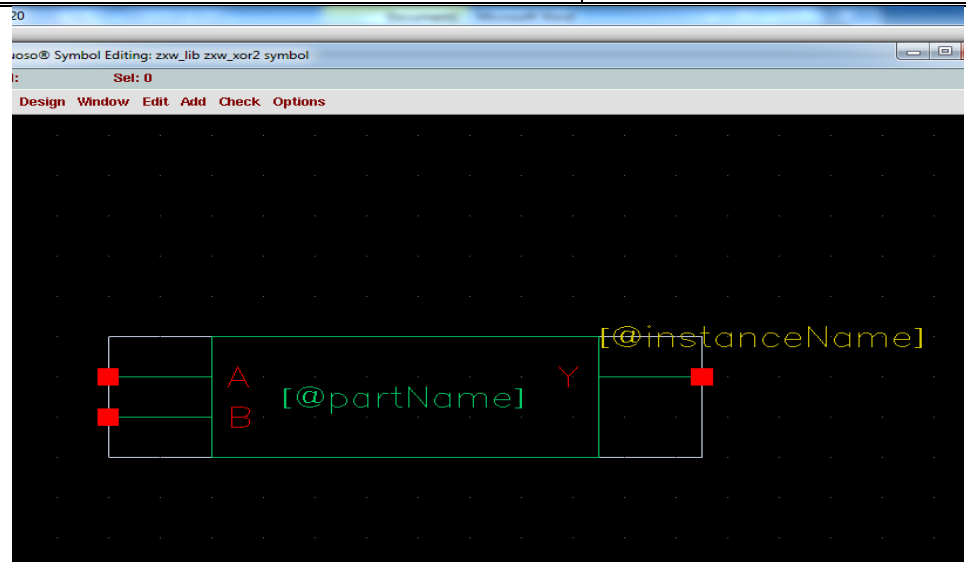

 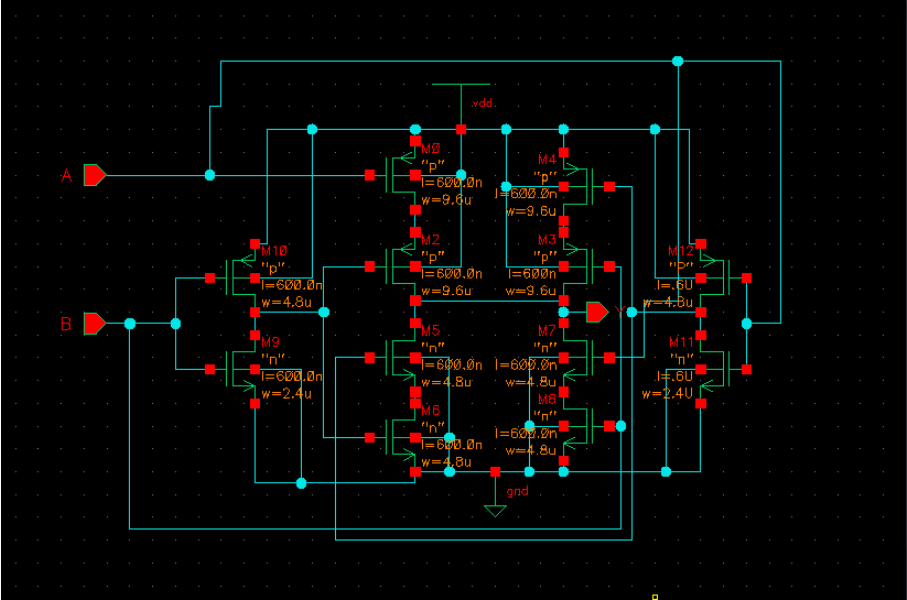

Layout 2776.8 um²

```
module zxw_xor2 (A,B,Y );
```

```
    input A,B;
```

```
    output Y;
```

```
    xor(Y,A,B);
```


endmodule

```
zxw_xor2.sp = (~/ee620) - GVIEW
File Edit Tools Syntax Buffers Window Help
SUBCKT zxw_xor2 vdd! gnd! A B Y
*
* caps2d version: 7
*
* TRANSISTOR CARDS
*
M11 net1#2 A#6 gnd!#6 gnd!#2 nmos L=0.6 W=2.4
+ AD=4.11 AS=4.11 PD=6.8 PS=6.8
M7 Y#4 A#7 net16#2 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.93 AS=6.9 PD=2.1 PS=8.6
M5 Y#4 net1#6 net17#2 gnd!#2 nmos L=0.6 W=4.8
+ AD=3.93 AS=6.9 PD=2.1 PS=8.6
M8 net16#4 B#3 gnd!#7 gnd!#2 nmos L=0.6 W=4.8
+ AD=6.9 AS=3.93 PD=8.6 PS=2.1
M6 net17#4 net5#2 gnd!#7 gnd!#2 nmos L=0.6 W=4.8
+ AD=6.9 AS=3.93 PD=8.6 PS=2.1
M9 net5#4 B#8 gnd!#1 gnd!#2 nmos L=0.6 W=2.4
+ AD=4.11 AS=4.11 PD=6.8 PS=6.8
M12 net1 A#8 vdd!#8 vdd!#2 pmos L=0.6 W=4.8
+ AD=6.79 AS=7.03 PD=8.4 PS=8.5
M0 net44 A#4 vdd!#7 vdd!#2 pmos L=0.6 W=9.6
+ AD=12.48 AS=7.2 PD=12.2 PS=1.5
M4 net33 net1#5 vdd!#7 vdd!#2 pmos L=0.6 W=9.6
+ AD=7.2 AS=7.2 PD=1.5 PS=1.5
M3 Y#3 B#1 net33 vdd!#2 pmos L=0.6 W=9.6
+ AD=7.2 AS=7.2 PD=1.5 PS=1.5
M2 Y#3 net5 net44#3 vdd!#2 pmos L=0.6 W=9.6
+ AD=7.2 AS=12.48 PD=1.5 PS=12.2
M10 net5#6 B#6 vdd!#1 vdd!#2 pmos L=0.6 W=4.8
+ AD=6.79 AS=6.79 PD=8.4 PS=8.4
*
* RESISTOR AND CAP/DIODE CARDS
*
Re1 A#4 A#5 424.8754
Re2 A#5 A#1 75.9090
Re3 A#1 A#6 225.7579
Re4 A#5 A#7 198.8517
Re5 A#1 A#8 203.0000
Re6 net1#5 net1#6 626.0237
Re7 net1#6 net1#4 584.4108
Re8 B#1 B#2 350.8333
Re9 B#2 B#3 185.0000
Re10 B#6 B#7 422.0797
Re11 B#7 B#8 241.2903
```

zxw_DFF

clk	Set	D	Q	Qbar
0	0	-	1	0
0	1	-	0	1
0 to 1	1	1	1	0
0 to 1	1	0	0	1

Phi1 Q↑	2.04ns
Phi1 Q↓	2.98ns
Phi1 Qbar↑	1.87ns
Phi1 Qbar↓	1.94ns
Phi1 minimum pulse width	450ps
Phi2 minimum pulse width	440ps
Guard time	1ps

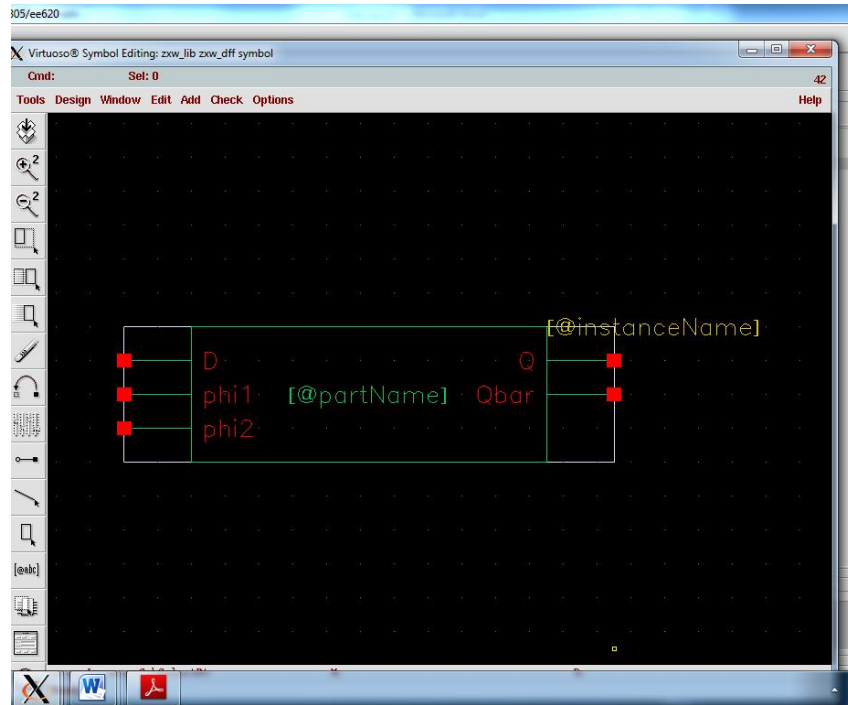



atic Editing: zxw_lib zxw_dff schematic

Sel: 0

ndow Edit Add Check Sheet Options Migrate

He

 

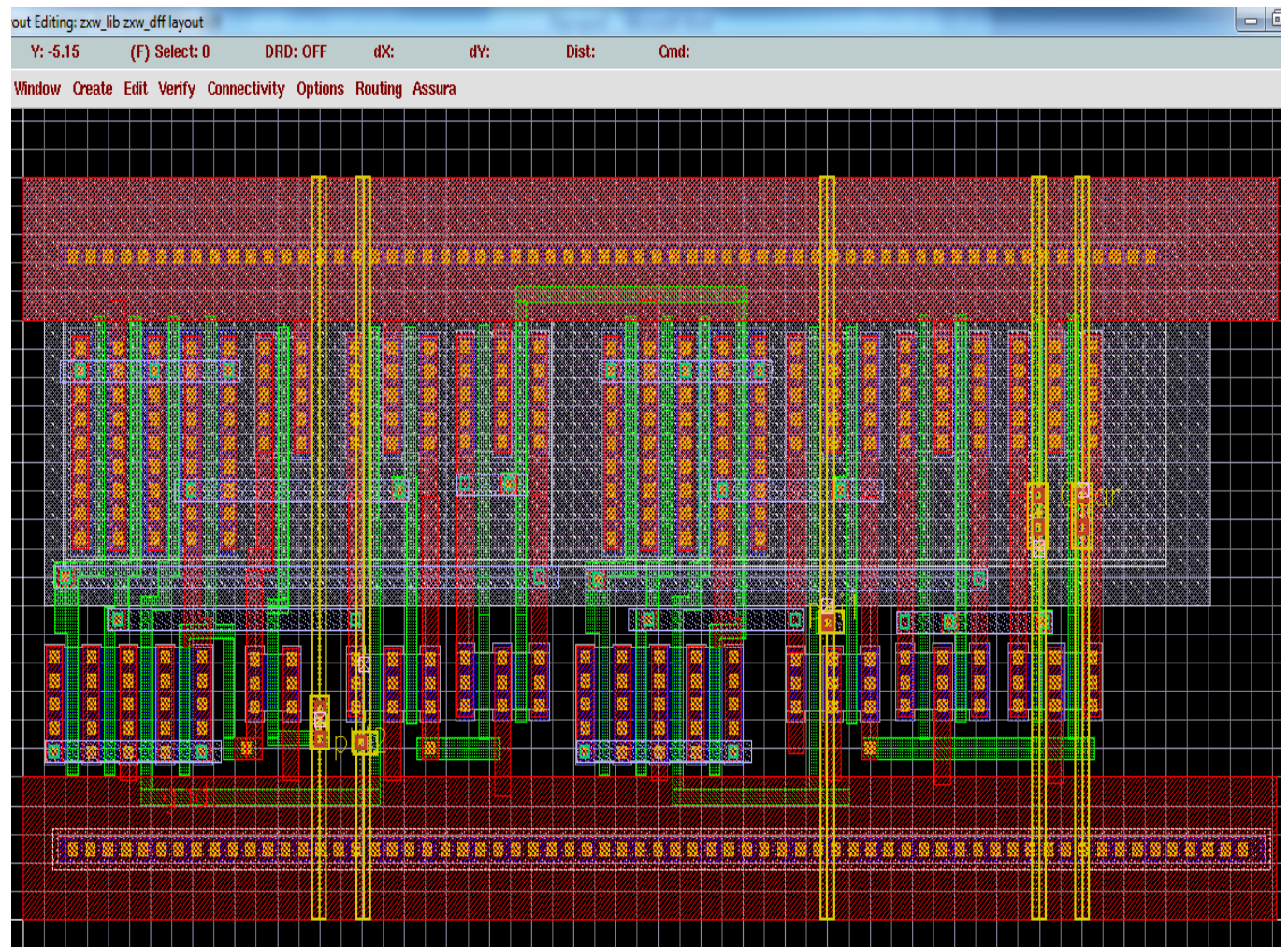

Layout 2096.6 um²

```

module zwx_dff ( Q, Qbar, D,phi2,phi1 );

    input D,phi2,phi1;

    output Q,Qbar;

    not(A,D);

    not(s2,phi2);

    fand(and1,s2,C);           // in2 is not feedback inverter

```



```
and(and2,phi2,A); // in3 is D
```

```
or (Y,and1,and2);
```

```
not(B,Y);
```

```
not(C,B);
```

```
not(s1,phi1);
```

```
and(and3,s1,E);
```

```
and(and4,phi1,B);
```

```
or(Z,and3,and4);
```

```
not(D,Z);
```

```
not(E,D);
```

```
not(Qbar,Z);
```

```
not(Q,D);
```



```
endmodule
```


```

zxw_dff.sp = (~/ee620) - GVIEW2
File Edit Tools Syntax Buffers Window Help
. SUBCKT zxw_dff gnd! D Q Qbar phi1 phi2
*
*
* caps2d version: 7
*
* TRANSISTOR CARDS
*
M50 net0183#2 net0346#4 net0268 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M51 net0268 net076#4 gnd!#16 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M49 net0260 phi1#5 gnd!#16 gnd!#1 nmos L=0.6 W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M48 net0183#3 net0130#6 net0260 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M10 net076#7 phi1#4 gnd!#15 gnd!#1 nmos L=0.6 W=2.4
+ AD=4 AS=2.24 PD=6.6 PS=2.3
M36 net0255#2 net0183#11 gnd!#15 gnd!#1 nmos L=0.6
+ W=2.4
+ AD=4 AS=2.24 PD=6.6 PS=2.3
M27 net0261#3 net0255#8 gnd!#14 gnd!#1 nmos L=0.6
+ W=2.4
+ AD=4.11 AS=2.295 PD=6.8 PS=2.4
M26 net0346#7 net0261#8 gnd!#14 gnd!#1 nmos L=0.6
+ W=2.4
+ AD=4.11 AS=2.295 PD=6.8 PS=2.4
M31 Q#3 net0261#11 gnd!#13 gnd!#1 nmos L=0.6 W=2.4
+ AD=4.11 AS=2.295 PD=6.8 PS=2.4
M30 Qbar#3 net0255#6 gnd!#13 gnd!#1 nmos L=0.6 W=2.4
+ AD=4.11 AS=2.295 PD=6.8 PS=2.4
M45 net0187#2 net0286#4 net0216 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M46 net0216 net0220#4 gnd!#12 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M44 net0208 phi2#6 gnd!#12 gnd!#1 nmos L=0.6 W=4.8
+ AD=3.765 AS=3.765 PD=1.8 PS=1.8
M43 net0187#3 net0211#3 net0208 gnd!#1 nmos L=0.6
+ W=4.8
+ AD=6.57 AS=3.765 PD=8 PS=1.8
M20 net0211#6 D#4 gnd!#19 gnd!#1 nmos L=0.6 W=2.4
+ AD=4 AS=4 PD=6.6 PS=6.6

```


BSC cell

 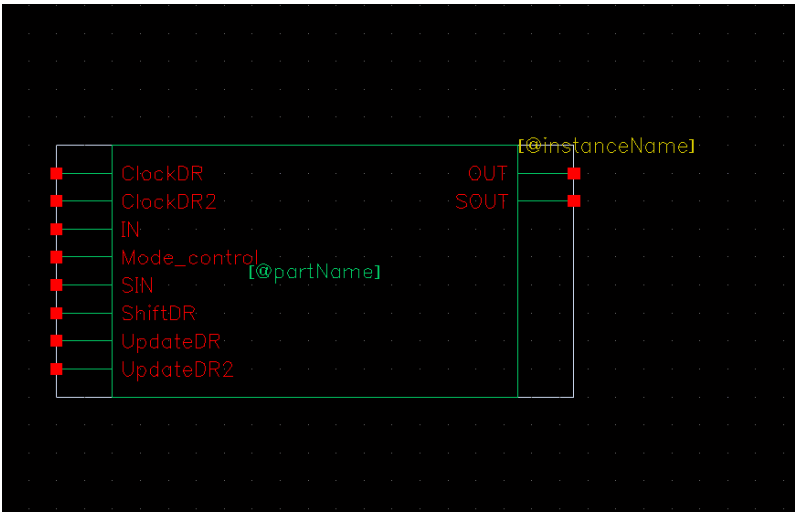


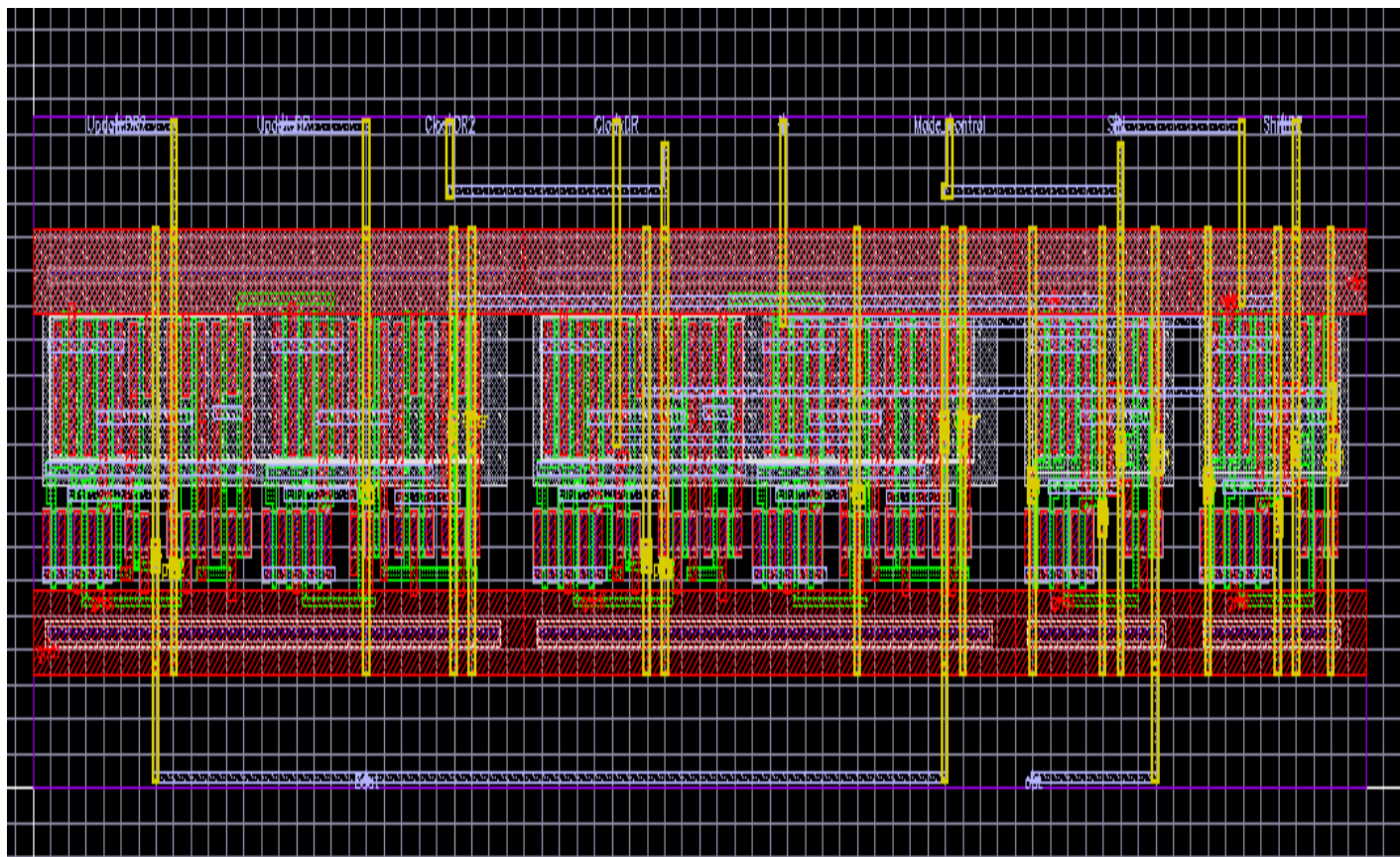


Layout 8534 um²

BSR5


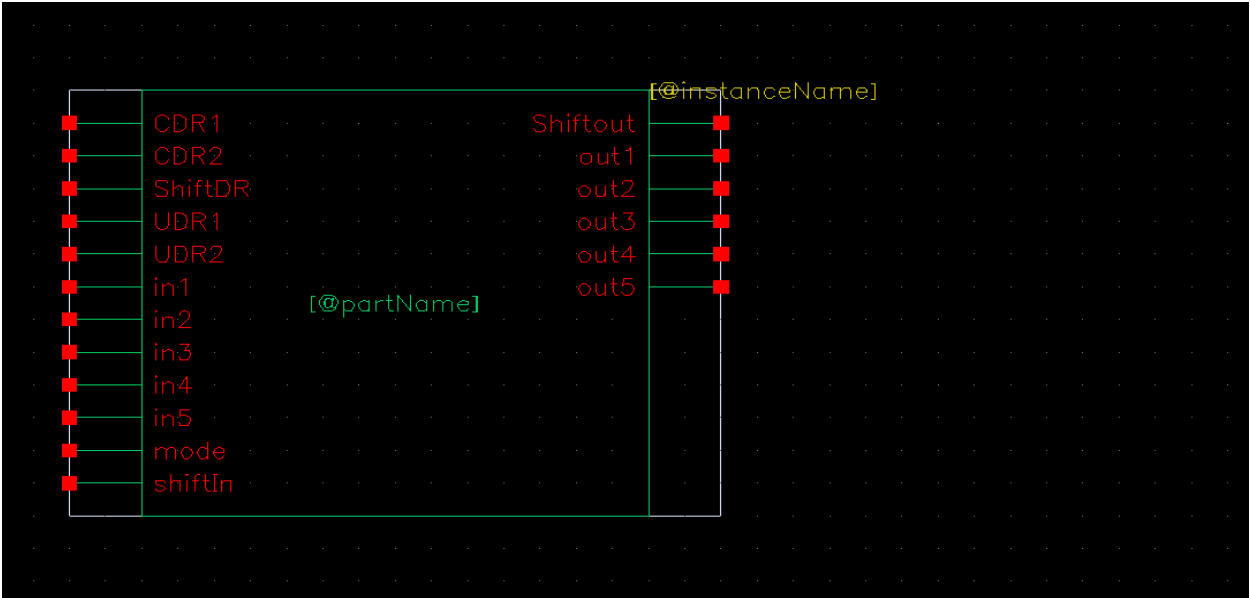


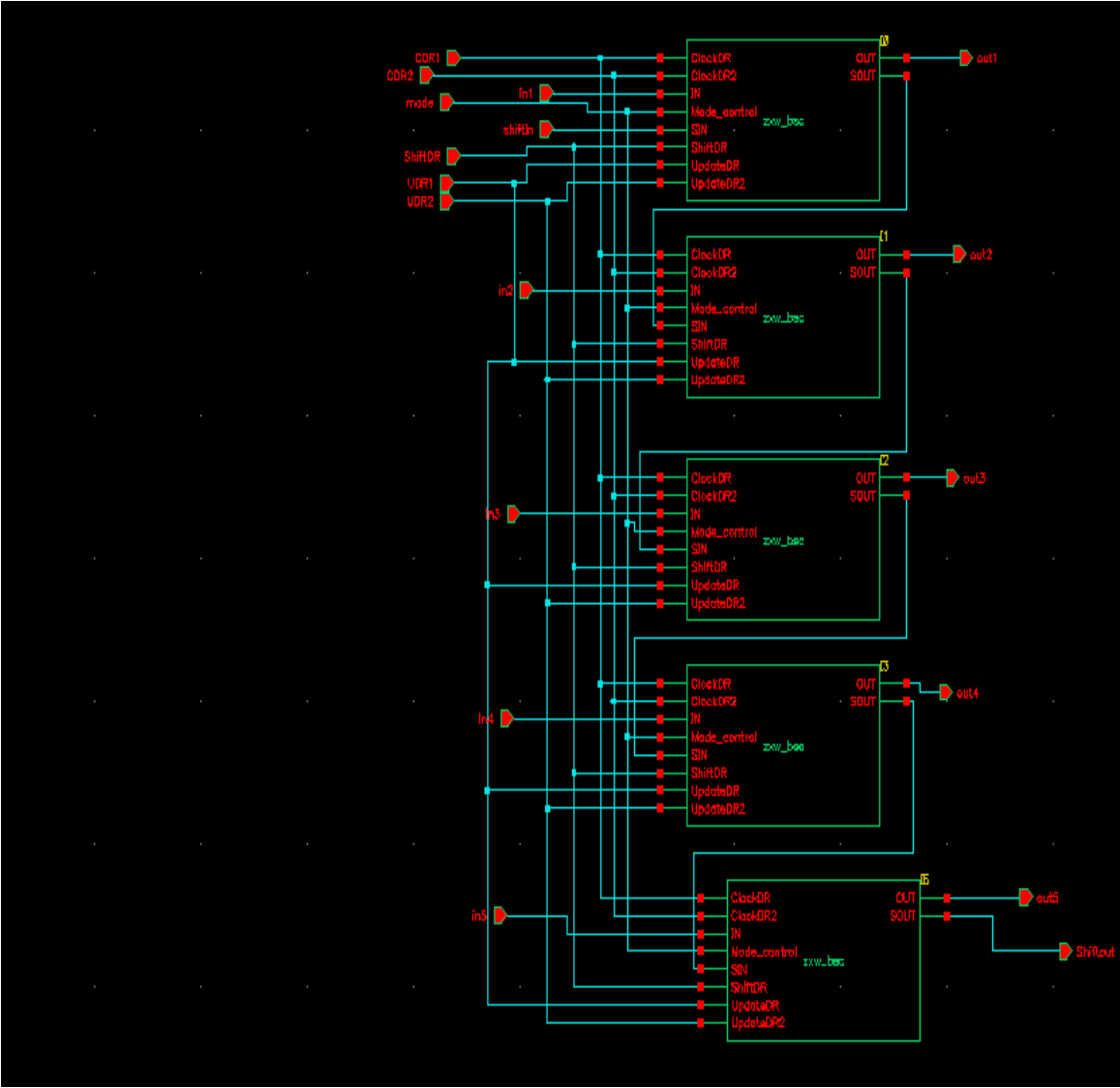

 


Layout 76310.5 μm^2

BSSUM

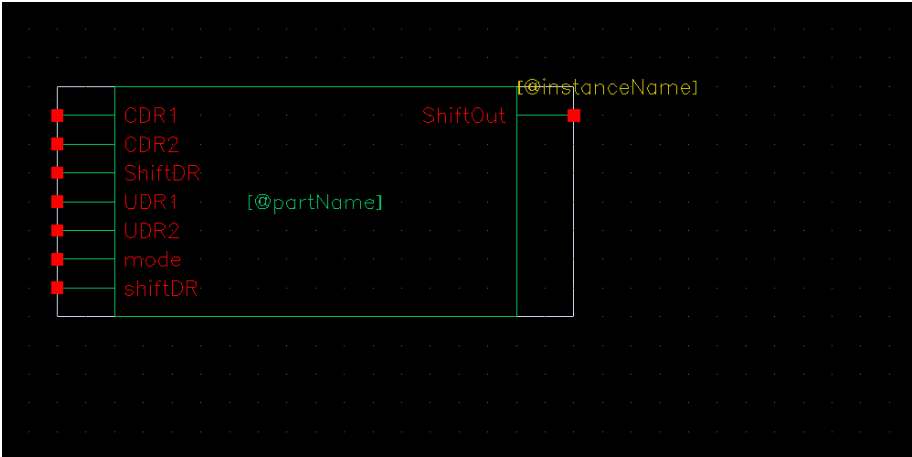
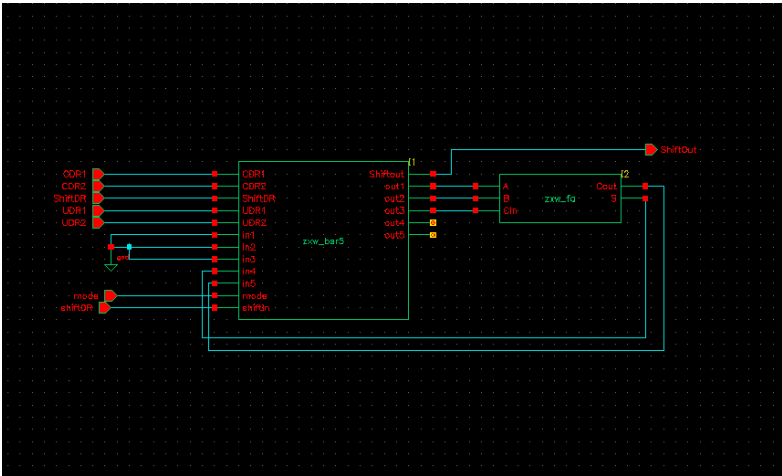



Layout 8534 um^2

 

Layout 95639.6um^2

BSTEST

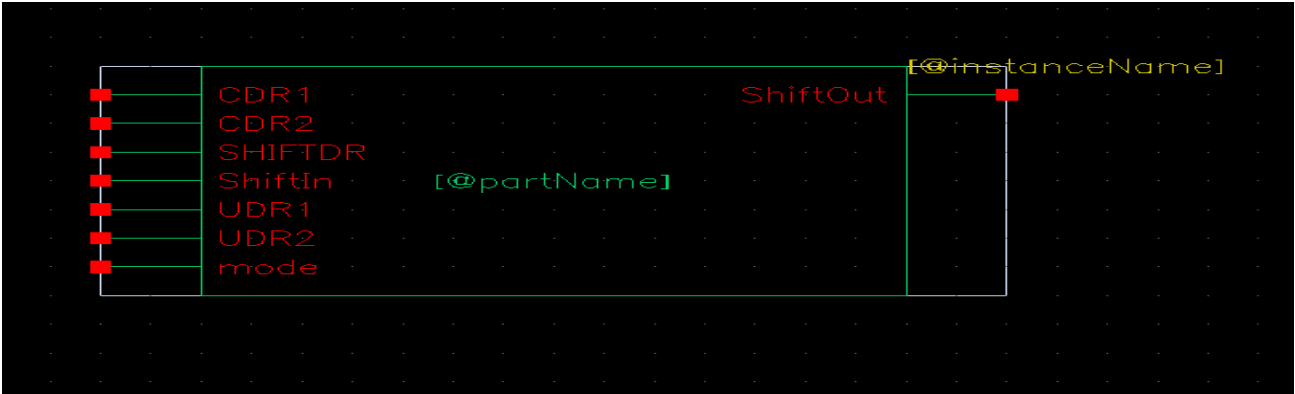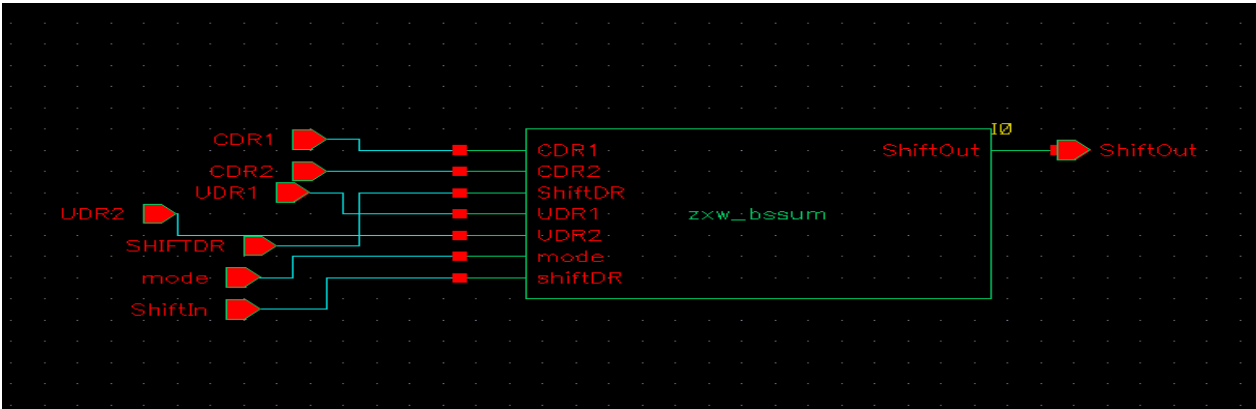

 

Layout 563475 um²